

---


# CSE477 VLSI Digital Circuits Spring 2004

## Lecture 04: CMOS Inverter (static view)

Yuan Xie ( [www.cse.psu.edu/~yuanxie](http://www.cse.psu.edu/~yuanxie) )  
[www.cse.psu.edu/~cg477](http://www.cse.psu.edu/~cg477)


[Adapted from Rabaey's *Digital Integrated Circuits*, Second Edition, ©2003  
J. Rabaey, A. Chandrakasan, B. Nikolic]

# Review: Design Abstraction Levels

 


# Review: The MOS Transistor


---

 


# CMOS Inverter: A First Look

 


# CMOS Inverter: Steady State Response

 


$$V_{out} = 1$$

 

$$V_{in} = 0$$

 

$$V_{out} = 0$$

 

$$V_{in} = V_{DD}$$


$$\boxed{V_{OL} = 0 \\ V_{OH} = V_{DD} \\ V_M = f(R_n, R_p)}$$

# CMOS Properties

---

- ❑ Full rail-to-rail swing  $\Rightarrow$  high noise margins
  - Logic levels not dependent upon the relative device sizes  $\Rightarrow$  transistors can be minimum size  $\Rightarrow$  ratioless
- ❑ Always a path to  $V_{dd}$  or GND in steady state  $\Rightarrow$  low output impedance (output resistance in  $k\Omega$  range)  $\Rightarrow$  large fan-out (albeit with degraded performance)
- ❑ Extremely high input resistance (gate of MOS transistor is near perfect insulator)  $\Rightarrow$  nearly zero steady-state input current
- ❑ No direct path steady-state between power and ground  $\Rightarrow$  no static power dissipation
- ❑ Propagation delay is a function of load capacitance and resistance of transistors


# Review: Short Channel I-V Plot (NMOS)

 

NMOS transistor,  $0.25\mu m$ ,  $L_d = 0.25\mu m$ ,  $W/L = 1.5$ ,  $V_{DD} = 2.5V$ ,  $V_T = 0.4V$
 
## Review: Short Channel I-V Plot (PMOS)

- All polarities of all voltages and currents are reversed



PMOS transistor,  $0.25\mu m$ ,  $L_d = 0.25\mu m$ ,  $W/L = 1.5$ ,  $V_{DD} = 2.5V$ ,  $V_T = -0.4V$




# Transforming PMOS I-V Lines

- Want common coordinate set  $V_{in}$ ,  $V_{out}$ , and  $I_{Dn}$


$$I_{DSp} = -I_{DSn}$$

$$V_{GSn} = V_{in} ; V_{GSp} = V_{in} - V_{DD}$$
   
$$V_{DSn} = V_{out} ; V_{DSP} = V_{out} - V_{DD}$$



 
$$V_{in} = V_{DD} + V_{GSp}$$
$$I_{Dn} = -I_{Dp}$$




$$V_{out} = V_{DD} + V_{DSP}$$

# CMOS Inverter Load Lines

 


0.25um,  $W/L_n = 1.5$ ,  $W/L_p = 4.5$ ,  $V_{DD} = 2.5V$ ,  $V_{Tn} = 0.4V$ ,  $V_{Tp} = -0.4V$



# CMOS Inverter VTC

 



# CMOS Inverter VTC

 
  
# CMOS Inverter: Switch Model of Dynamic Behavior


  
# CMOS Inverter: Switch Model of Dynamic Behavior



- Gate response time is determined by the time to charge  $C_L$  through  $R_p$  (discharge  $C_L$  through  $R_n$ )

# Relative Transistor Sizing

- ❑ When designing static CMOS circuits, balance the driving strengths of the transistors by making the PMOS section wider than the NMOS section to
  - maximize the noise margins and
  - obtain symmetrical characteristics

# Switching Threshold

- ❑  $V_M$  where  $V_{in} = V_{out}$  (both PMOS and NMOS in saturation since  $V_{DS} = V_{GS}$ )

$$V_M \approx rV_{DD}/(1 + r) \text{ where } r = k_p V_{DSATp}/k_n V_{DSATn}$$

- ❑ Switching threshold set by the ratio  $r$ , which compares the **relative driving strengths** of the PMOS and NMOS transistors

- ❑ Want  $V_M = V_{DD}/2$  (to have comparable high and low noise margins), so want  $r \approx 1$

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k_n' V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k_p' V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp}/2)}$$

# Switch Threshold Example

---

- In our generic 0.25 micron CMOS process, using the process parameters from slide L03.26, a  $V_{DD} = 2.5V$ , and a 1.5 size NMOS device  $(W/L)_n$

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	$115 \times 10^{-6}$	0.06
PMOS	-0.4	-0.4	-1	$-30 \times 10^{-6}$	-0.1

$$\frac{(W/L)_p}{(W/L)_n} =$$

## Switch Threshold Example


- In our generic 0.25 micron CMOS process, using the process parameters from slide L03.26, a  $V_{DD} = 2.5V$ , and a 1.5 size NMOS device  $(W/L)_n$

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	$115 \times 10^{-6}$	0.06
PMOS	-0.4	-0.4	-1	$-30 \times 10^{-6}$	-0.1

$$\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6}}{-30 \times 10^{-6}} \times \frac{0.63}{-1.0} \times \frac{(1.25 - 0.43 - 0.63/2)}{(1.25 - 0.4 - 1.0/2)} = 3.5$$

$$(W/L)_p = 3.5 \times 1.5 = 5.25 \text{ for a } V_M \text{ of } 1.25V$$


# Simulated Inverter $V_M$

 

Note: x-axis is semilog

- ❑  $V_M$  is relatively insensitive to variations in device ratio
  - setting the ratio to 3, 2.5 and 2 gives  $V_M$ 's of 1.22V, 1.18V, and 1.13V
- ❑ Increasing the width of the PMOS moves  $V_M$  towards  $V_{DD}$
- ❑ Increasing the width of the NMOS moves  $V_M$  toward GND
 
# Noise Margins Determining $V_{IH}$ and $V_{IL}$



By definition,  $V_{IH}$  and  $V_{IL}$  are where  $dV_{out}/dV_{in} = -1$  (= gain)

$$NM_H = V_{DD} - V_{IH}$$
$$NM_L = V_{IL} - GND$$


Approximating:

$$V_{IH} = V_M - V_M/g$$

$$V_{IL} = V_M + (V_{DD} - V_M)/g$$

So high gain in the transition region is very desirable

# Gain Determinates

 


Gain is a strong function of the slopes of the currents in the saturation region, for  $V_{in} = V_M$

$$g \approx \frac{(1+r)}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

Determined by technology parameters, especially channel length modulation ( $\lambda$ ). Only designer influence through **supply voltage** and  $V_M$  (**transistor sizing**).

# CMOS Inverter VTC from Simulation

 

$0.25\text{um}, (W/L)_p/(W/L)_n = 3.4$   
 $(W/L)_n = 1.5$  (min size)  
 $V_{DD} = 2.5\text{V}$

$V_M \approx 1.25\text{V}, g = -27.5$

$V_{IL} = 1.2\text{V}, V_{IH} = 1.3\text{V}$

$NM_L = NM_H = 1.2$


(actual values are

$V_{IL} = 1.03\text{V}, V_{IH} = 1.45\text{V}$

$NM_L = 1.03\text{V} \& NM_H = 1.05\text{V}$ )



Output resistance  
low-output =  $2.4\text{k}\Omega$   
high-output =  $3.3\text{k}\Omega$
 
# Impact of Process Variation on VTC Curve




- Process variations (mostly) cause a shift in the switching threshold

# Scaling the Supply Voltage

  

# Project Partner

# Next Time: CMOS Inverter *max* Layout

 

# Next Lecture and Reminders

---

## ❑ Next lecture

- IC manufacturing
  - Reading assignment – Rabaey, et al, 2.1-2.3

## ❑ Reminders

- HW1 due today, HW2 is out and due on Feb 10
- Project team and title due Jan 27 (**next class!**)