

Balanced Three-Phase Systems

Three-Phase Generator

e_{AN} , e_{BN} , e_{CN} : Induced Voltages of 3-phase generator


$$e_{AN} = E_m \sin(\omega t)$$

$$e_{BN} = E_m \sin(\omega t - 120^\circ)$$

$$e_{CN} = E_m \sin(\omega t - 240^\circ)$$


The phasor diagram:
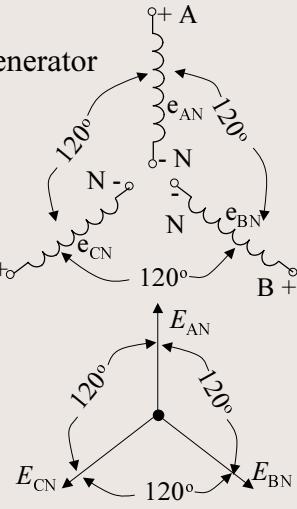
$$\begin{aligned} \text{Phasor form of phase voltages} & \left\{ \begin{array}{l} E_{AN} = E_{BN} = E_{CN} = E_{rms} \\ \bar{E}_{AN} = E_{rms} \angle 0^\circ \\ \bar{E}_{BN} = E_{rms} \angle -120^\circ \\ \bar{E}_{CN} = E_{rms} \angle +120^\circ \\ \bar{E}_{AN} + \bar{E}_{BN} + \bar{E}_{CN} = 0 \end{array} \right. \end{aligned}$$





1



The Y-Connected Generator

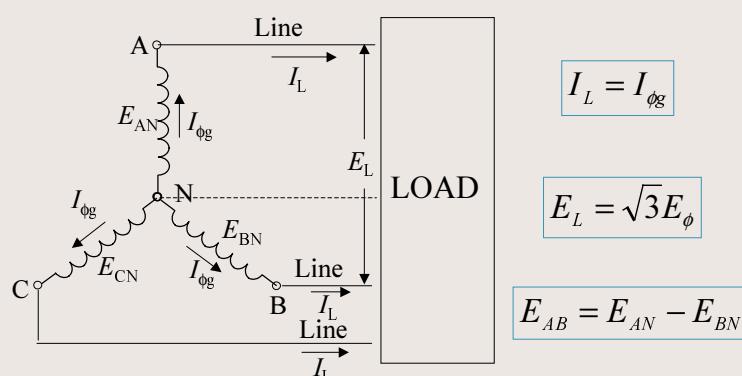

- The point at which all the points are connected is called the neutral point.
- Y-connected 3φ, 3-wire
- Y-connected 3φ, 4-wire (neutral connected)

2

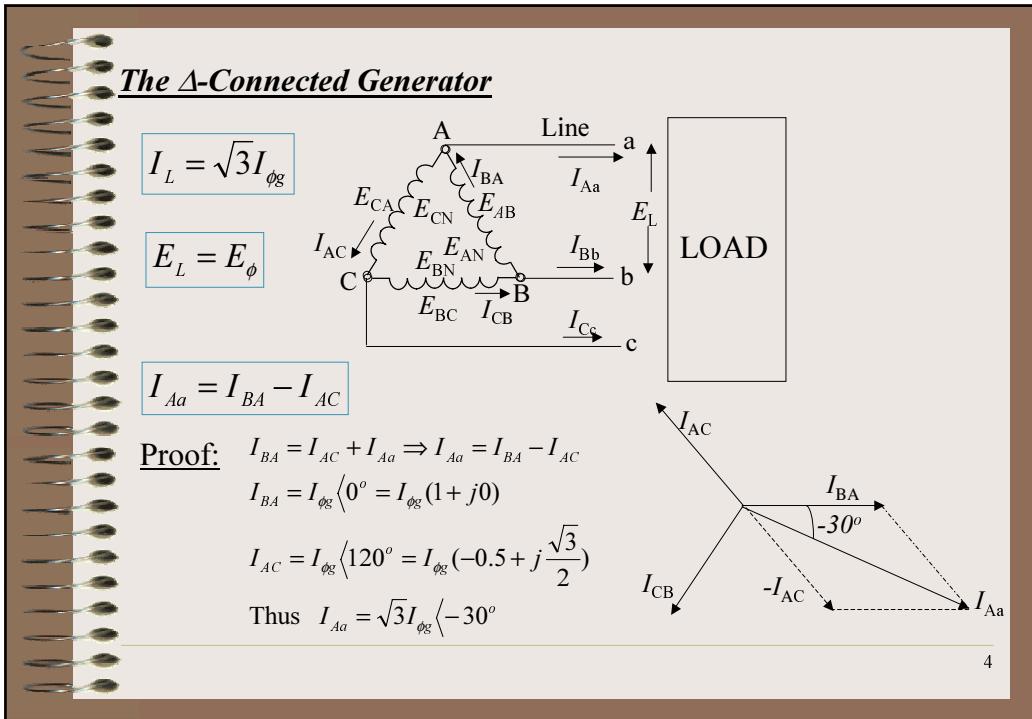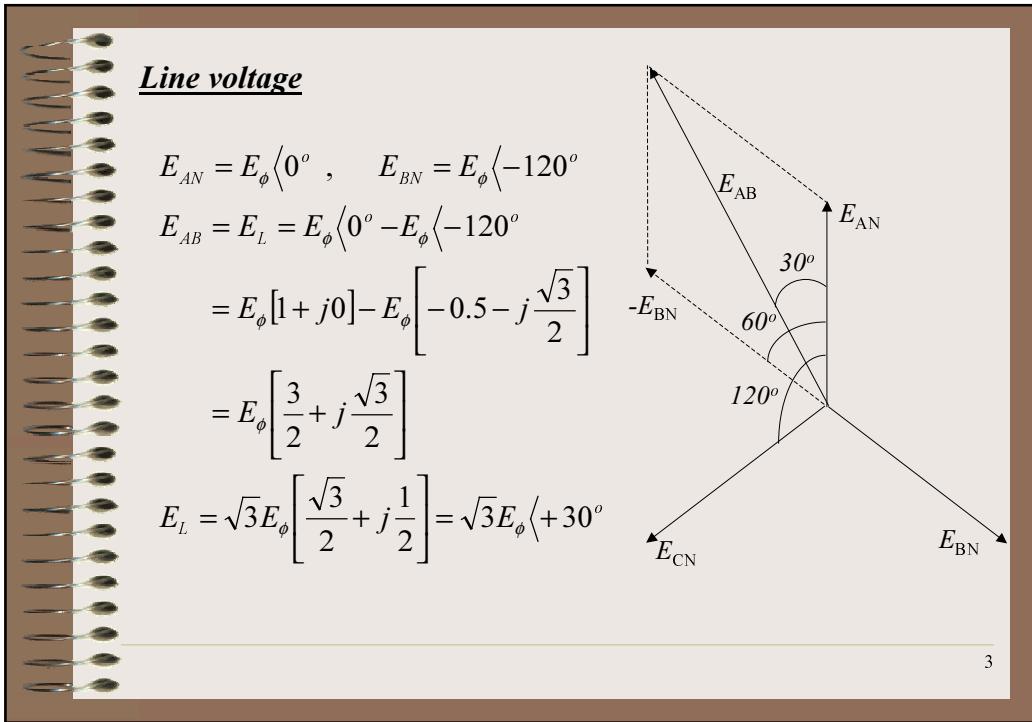

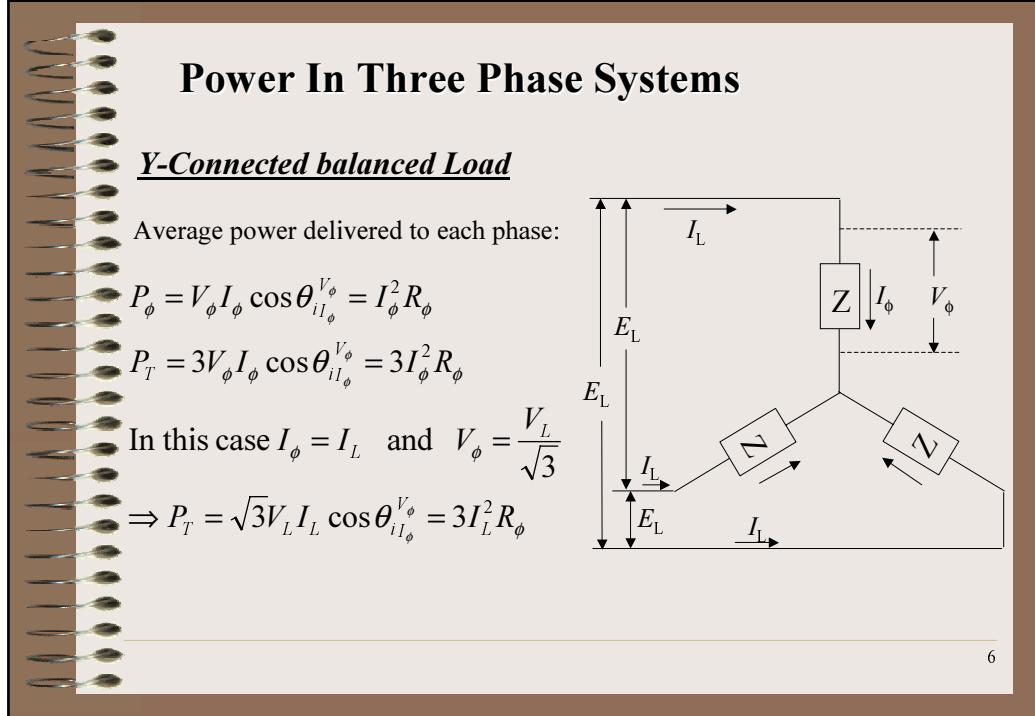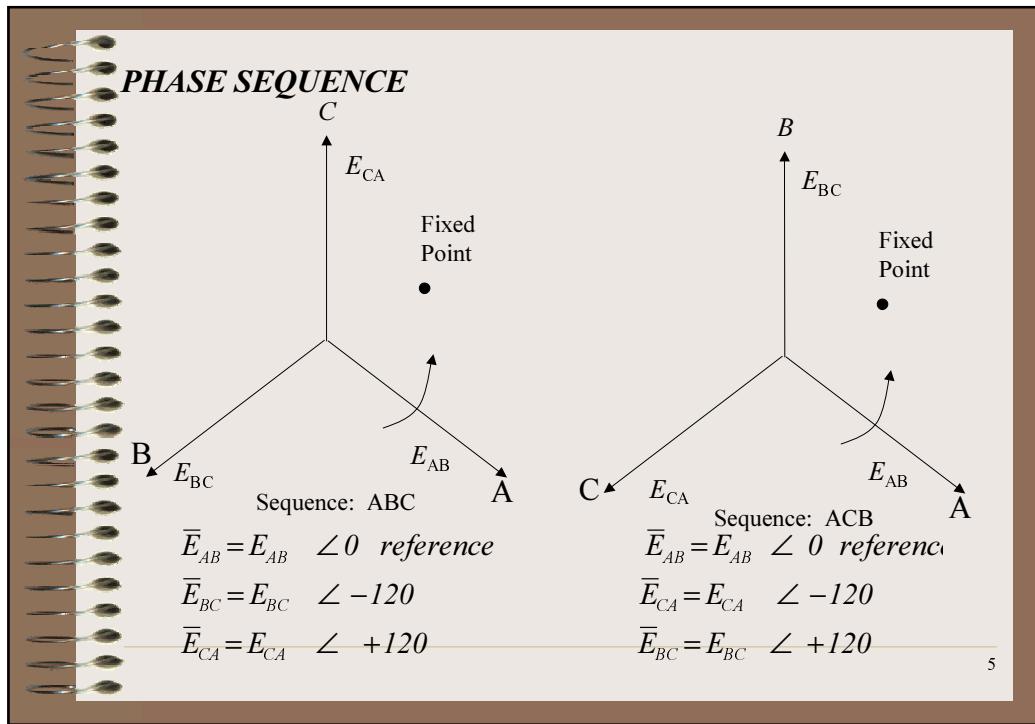

Δ -Connected balanced Load


Average power delivered to each phase:

$$P_\phi = V_\phi I_\phi \cos \theta_{iI_\phi} = I_\phi^2 R_\phi = \frac{V_R^2}{R_\phi}$$

$$P_T = 3P_\phi$$

$$\text{In this case } I_\phi = \frac{I_L}{\sqrt{3}} \text{ and } V_\phi = V_L$$
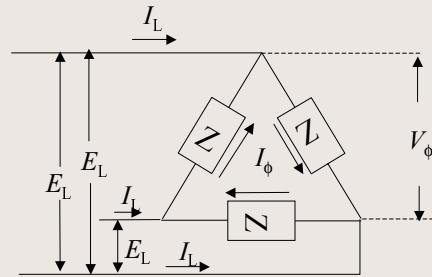
$$\Rightarrow P_T = \sqrt{3}V_L I_L \cos \theta_{iI_\phi} = 3I_L^2 R = \frac{3V_R^2}{R_\phi}$$




7

Power Measurement In 3 Phase Systems

The 3 Wattmeter Method


$$\text{Y-Connected, 4 Wire Load: } P_{TY} = P_1 + P_2 + P_3$$

$$P_{T\Delta} = P_1 + P_2 + P_3$$

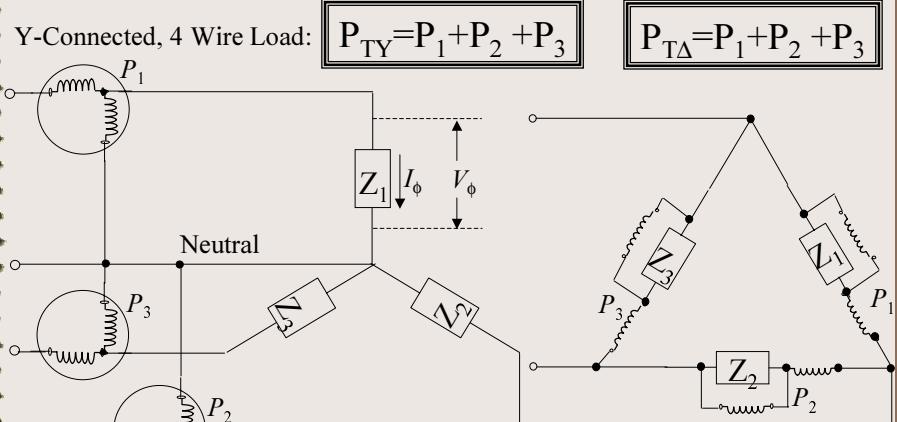

8

The 2 Wattmeter Method

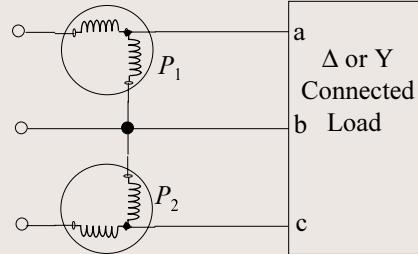


$$P_T = P_1 + P_2$$

$$P_1 = I_a V_{ab} \cos \theta_1 = V_L I_L \cos(\theta + 30^\circ)$$


$$P_2 = I_c V_{cb} \cos \theta_2 = V_L I_L \cos(\theta - 30^\circ)$$
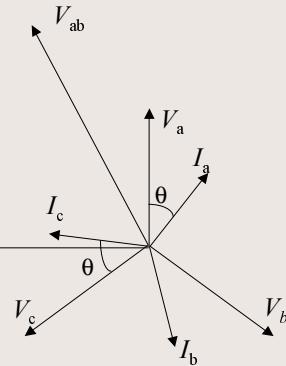
$$P_T = P_1 + P_2 = \sqrt{3} V_L I_L \cos(\theta)$$



9

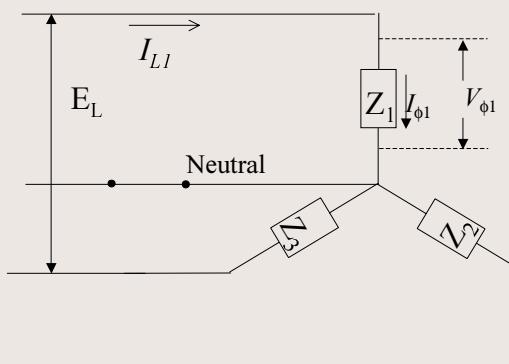Unbalance 3-Phase, Four-wire, Y-Connected Load



$$V_\phi = E_\phi, \quad I_{\phi l} = I_{Ll} = \frac{V_{\phi l}}{Z_l}, \quad I_N = I_{\phi l} + I_{\phi 2} + I_{\phi 3}$$

10

